

ELECENG 3EJ4

Lab Report #1

Instructor: Dr. Chen

Jasmine Dosanjh – dosanj5 – 400531879

September 21, 2025

Part 1 Questions

Q1. (7 Points)

V+ (VCC)	V- (VE)	V(Q1C) (Volt)	V(Q1B) (Volt)	VCE (Volt)	VBEn (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = I_C/I_B$	VA (V)	ro=VA/IC	gm = IC/25mV	r π = 25mV/IB
0.5	-1.5	0.397558296	-0.878689331	1.898	0.621	100	1.00E+05	1.02E-03	8.79E-06	117	1000	9.76E+05	4.10E-02	2845

(1) $V_{BEon} = 0.621V, I_B = 8.79 \times 10^{-6}A = 8.79\mu A$

(2) $\beta = 117$

(3) $|V_A| = 1000V$

(4) $r_o = 9.76 \times 10^5 \Omega \times \frac{1k\Omega}{10^3 \Omega} = 9.76 \times 10^2 k\Omega = 976k\Omega$

(5) $g_m = 4.1 \times 10^{-2} S \times \frac{1mS}{10^{-3} S} = 41mS$

(6) $r_\pi = 2845 \Omega \times \frac{1k\Omega}{10^3 \Omega} = 2.845k\Omega$

Q2. (8 Points)

V+ (VCC)	V- (VE)	V(Q1C) (Volt)	V(Q1B) (Volt)	VCE (Volt)	VBEn (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = I_C/I_B$	VA (V)	ro=VA/IC	gm = IC/25mV	r π = 25mV/IB
1	-1.5	0.76768	-0.82146	2.26768	0.67854	100	1.00E+05	2.32E-03	8.21E-06	283	55	2.73E+04	9.29E-02	3043

(1) $I_C = 2.32 \times 10^{-3}A = 2.32mA$

(2) $V_{BEon} = 0.67854V, I_B = 8.21 \times 10^{-6}A = 8.21\mu A$

(3) $\beta = 283$

(4) $|V_A| = 55V$

(5) $r_o = 2.73 \times 10^4 \Omega \times \frac{1k\Omega}{10^3 \Omega} = 2.73 \times 10^1 k\Omega = 27.3k\Omega$

(6) $g_m = 9.29 \times 10^{-2} S \times \frac{1mS}{10^{-3} S} = 92.9mS$

(7) $r_\pi = 3043 \Omega \times \frac{1k\Omega}{10^3 \Omega} = 3.043k\Omega$

Part 2 Questions

Q3. (7 Points)

V+ (VE)	V- (VCC)	V(Q1C) (Volt)	V(Q1B) (Volt)	VEC (Volt)	VEBon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = IC/IB$	VA (V)	ro=VA/IC	gm = IC/25mV	r π = 25mV/IB
1.5	-0.5	-0.39709332	0.839935339	1.90	0.660	100	1.00E+05	1.03E-03	8.40E-06	123	143	1.39E+05	4.12E-02	2976

(1) $V_{BEon} = 0.660V, I_B = 8.40 \times 10^{-6}A = 8.40\mu A$

(2) $\beta = 123$

(3) $|V_A| = 143V$

(4) $r_o = 1.39 \times 10^5 \Omega \times \frac{1k\Omega}{10^3 \Omega} = 1.39 \times 10^2 k\Omega = 139k\Omega$

(5) $g_m = 4.12 \times 10^{-2} S \times \frac{1mS}{10^{-3} S} = 41.2mS$

(6) $r_\pi = 2976 \Omega \times \frac{1k\Omega}{10^3 \Omega} = 2.976k\Omega$

Q4. (8 Points)

V+ (VE)	V- (VCC)	V(Q1C) (Volt)	V(Q1B) (Volt)	VEC (Volt)	VEBon (Volt)	RC (ohm)	RB (ohm)	IC (A)	IB (A)	$\beta = IC/IB$	VA (V)	ro=VA/IC	gm = IC/25mV	r π = 25mV/IB
1.5	-0.5	-0.09822	0.899	1.60	0.601	100	1.00E+05	4.02E-03	8.99E-06	447	19	4.73E+03	1.61E-01	2781

(1) $I_C = 4.02 \times 10^{-3}A = 4.02mA$

(2) $V_{BEon} = 0.601V, I_B = 8.99 \times 10^{-6}A = 8.99\mu A$

(3) $\beta = 447$

(4) $|V_A| = 19V$


(5) $r_o = 4.73 \times 10^3 \Omega \times \frac{1k\Omega}{10^3 \Omega} = 4.73k\Omega$

(6) $g_m = 1.61 \times 10^{-1} S \times \frac{1mS}{10^{-3} S} = 161mS$

(7) $r_\pi = 2781 \Omega \times \frac{1k\Omega}{10^3 \Omega} = 2.781k\Omega$

Part 3 Questions

Q5. (10 Points)

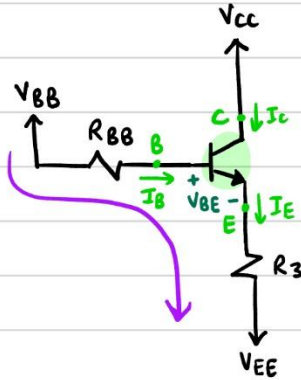

① Since BJT F.A.

(i) $V_{BE} = 0.7V$

(ii) $I_E = I_B + I_C$, $\therefore \beta = \frac{I_C}{I_B} \Rightarrow I_E = I_B + \beta I_B$

$\therefore I_E = (\beta + 1)I_B$

② Find a 3rd KVL eqn on a path that includes V_{BE} :

KVL: $V_{BB} - I_B R_{BB} - V_{BEon} - I_E R_3 = V_{EE}$ $I_E = (\beta + 1)I_B$

$V_{BB} - I_B R_{BB} - V_{BEon} - (\beta + 1)I_B R_3 = V_{EE}$

$V_{BB} - V_{EE} - V_{BEon} = (\beta + 1)I_B R_3 + I_B R_{BB}$

$V_{BB} - V_{EE} - V_{BEon} = I_B [(\beta + 1)R_3 + R_{BB}]$

$$I_B = \frac{V_{BB} - V_{EE} - V_{BEon}}{(\beta + 1)R_3 + R_{BB}}$$

Q6. (10 Points)

(i) Comparing I_B Expressions:

The main difference between equations 3 and 5 is the presence of R_3 . Equation (3) does not contain R_3 because it was set to 0. Therefore, equation 5 contains the additional term $(\beta + 1)R_3$.

$$I_B = \frac{V_{BB} - V_{EE} - V_{BEon}}{R_{BB}} \quad (3)$$

$$I_B = \frac{V_{BB} - V_{EE} - V_{BEon}}{(\beta + 1)R_3 + R_{BB}} \quad (5)$$

(ii) Deriving Equations:

Applying a change in power supply ΔV_{EE} to the equations above gives,


$$\Delta I_{B2} = \frac{V_{BB} - (V_{EE} + \Delta V_{EE2}) - V_{BEon}}{R_{BB}} \quad (3.1) \quad \Delta I_{B1} = \left[\frac{V_{BB} - (V_{EE} + \Delta V_{EE1}) - V_{BEon}}{(\beta + 1)R_3 + R_{BB}} \right] \quad (5.1)$$

In equation 3.1, the change in power supply is directly related to the change in current ($V_{EE2} \propto \Delta I_{B2}$).


Whereas the presence of R_3 in equation 5.1 reduces ΔI_{B1} because they are inversely proportional

$(I_{B1} \propto \frac{1}{R_3})$.

Q7. (15 Points)

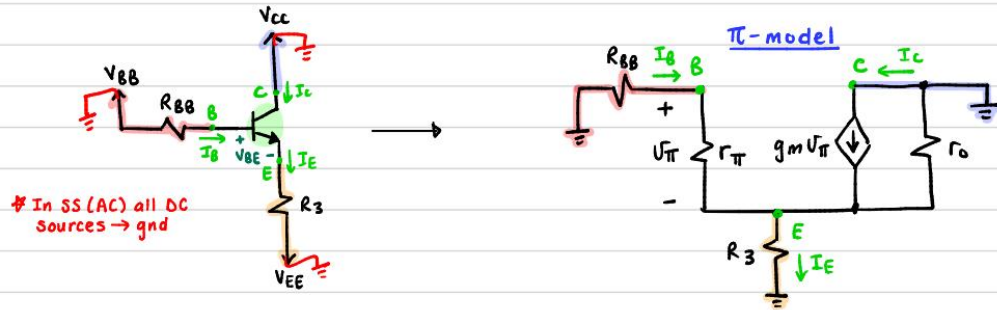

For g-parameters, $R_o = g_{22} = \frac{V_2}{I_2} \big|_{V_1=0}$

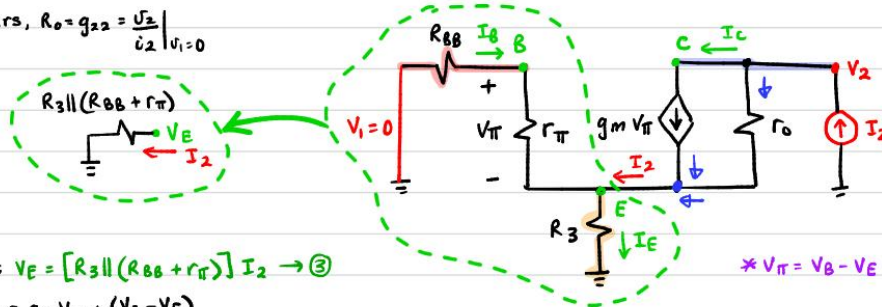

① Inspection: $V_E = [R_E || (R_{BB} + r_{\pi})] I_2 \rightarrow ③$

② Node C: $I_2 = g_m V_{\pi} + \frac{V_2 - V_E}{r_o}$
 $I_2 = g_m V_{\pi} + \frac{V_2}{r_o} - \frac{V_E}{r_o} \rightarrow ①$

③ Node B: $\frac{V_B}{R_{BB}} + \frac{(V_B - V_E)}{r_{\pi}} = 0$

$$\frac{V_B}{R_{BB}} + \frac{V_{\pi}}{r_{\pi}} = 0$$

$$V_B = -\frac{R_{BB}}{r_{\pi}} V_{\pi}$$

$$V_{\pi} + V_E = -\frac{R_{BB}}{r_{\pi}} V_{\pi}$$

$$V_{\pi} \left(1 + \frac{R_{BB}}{r_{\pi}}\right) = -V_E$$

$$V_{\pi} \left(\frac{r_{\pi} + R_{BB}}{r_{\pi}}\right) = -V_E$$

$$V_{\pi} = -V_E \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}}\right) \rightarrow ②$$

④ 2 in 1: $I_2 = g_m \left[-V_E \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right) \right] + \frac{V_2}{r_o} - \frac{V_E}{r_o}$

$$I_2 = -g_m V_E \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right) + \frac{V_2}{r_o} - \frac{V_E}{r_o}$$

$$\frac{V_2}{r_o} = I_2 + g_m V_E \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right) + \frac{V_E}{r_o}$$

$$\frac{V_2}{r_o} = I_2 + \overset{\text{sub ③}}{V_E} \left[g_m \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right) + \frac{1}{r_o} \right]$$

$$r_o \times \left(\frac{V_2}{r_o} = I_2 + [R_E || (R_{BB} + r_{\pi})] I_2 \left[g_m \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right) + \frac{1}{r_o} \right] \right)$$

$$V_2 = r_o I_2 + [R_E || (R_{BB} + r_{\pi})] I_2 \left[g_m \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right) + \frac{1}{r_o} \right] r_o$$

$$V_2 = I_2 \left[r_o + [R_E || (R_{BB} + r_{\pi})] \left[g_m \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right) + \frac{1}{r_o} \right] r_o \right]$$

$$\frac{V_2}{I_2} = r_o + [R_E || (R_{BB} + r_{\pi})] \left[g_m r_o \left(\frac{r_{\pi}}{r_{\pi} + R_{BB}} \right) + 1 \right]$$

Q8. (10 Points)

When $R_3 = 0$:

$$V_{o,min} = V_{EE} + 0.3V \quad (1)$$

Since $R_3 \neq 0$, the voltage drop across this resistor needs to be considered. Thus, an additional factor of $V_{R3} = I_E R_3$ will be added to (1) to give us a new expression:

$$V_{o,min} = V_{EE} + I_E R_3 + 0.3V$$

Since $I_C = \alpha I_E$ and $I_C = I_o$:

$$V_{o,min} = V_{EE} + \frac{I_o}{\alpha} R_3 + 0.3V \quad (2)$$

This is illustrated in the figures below:

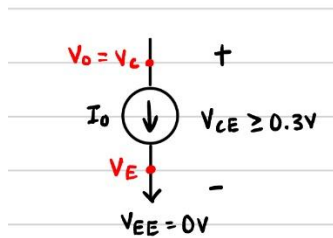


Fig 1. Ideal Current Sink when $R_3 = 0$

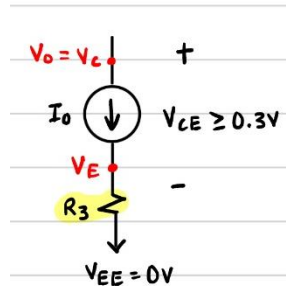


Fig 2. Ideal Current Sink when $R_3 \neq 0$

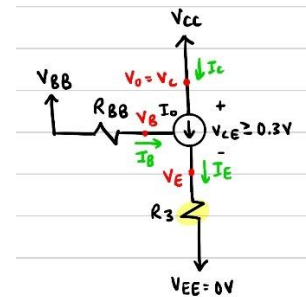


Fig 3. Real Current Sink when $R_3 \neq 0$

Q9. (15 Points)

(i) Finding R_3 :

$$\begin{aligned} \beta &= 117 \\ \alpha &= \frac{\beta}{\beta + 1} = \frac{117}{118} \\ V_{o,min} &= V_{EE} + \frac{I_o}{\alpha} R_3 + 0.3V \\ R_3 &= \left(V_{o,min} - V_{EE} - 0.3V \right) \frac{\alpha}{I_o} \\ &= [-1V - (-5V) - 0.3V] \left[\frac{117}{118} \cdot \frac{1}{(1mA)} \right] \\ R_3 &= 3.669k\Omega \end{aligned}$$

(ii) Finding R_1 :

KVL eqn from Q5:

$$V_{BB} - I_B R_{BB} - V_{BEon} - I_E R_3 = V_{EE}$$

$$\frac{R_1}{R_1 + R_2} V_{EE} - \frac{I_o}{\beta} \left(\frac{R_1 R_2}{R_1 + R_2} \right) - V_{BEon} - \frac{I_o}{\alpha} R_3 = V_{EE}$$

$$\frac{R_1}{R_1 + 100K} (-5V) - \frac{1mA}{117} \left(\frac{R_1 (100K)}{R_1 + 100K} \right) - 0.621 - 1mA \left(\frac{118}{117} \right) (3.669k\Omega) = -5V$$

$$\frac{-5R_1}{R_1 + 100K} - \frac{100}{117} \left(\frac{R_1}{R_1 + 100K} \right) - 0.621 - 3.7 = -5$$

$$\frac{-5R_1}{R_1 + 100K} - 0.854 \left(\frac{R_1}{R_1 + 100K} \right) = -0.679$$

$$\frac{-5R_1 - 0.854 R_1}{R_1 + 100K} = -0.679$$

$$-5R_1 - 0.854 R_1 = -0.679 (R_1 + 100K)$$

$$-5R_1 - 0.854 R_1 = -0.679 R_1 - 67.9K$$

$$R_1 (-5 - 0.854 + 0.679) = -67.9K$$

$$-5.175 R_1 = -67.9K$$

$$\boxed{R_1 = 13.12k\Omega}$$

(iii) Verifying I_o vs. V_{CC} characteristics:

Below is a graph of the I_o vs. V_{CC} characteristics and the PSpice Schematic used to generate them.

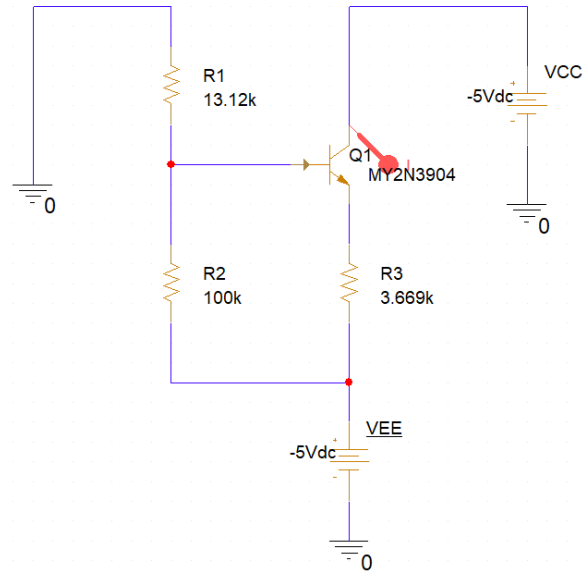


Fig 4. PSpice Schematic

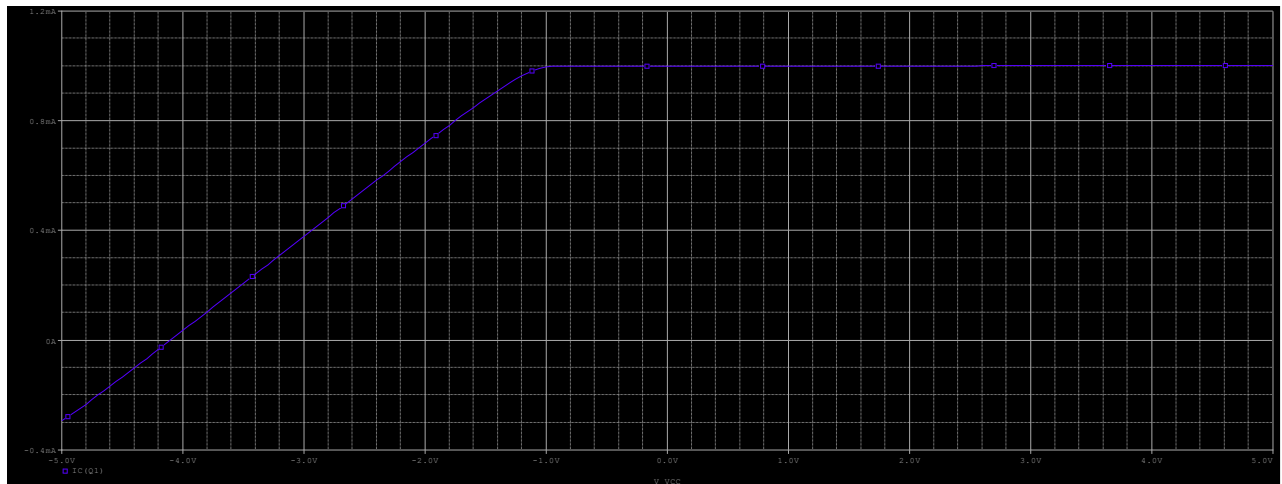


Fig 5. I_o vs. V_{CC} characteristics

From Figure 5, it shows that when $V_{CC} = -1V = V_{o,min}$, I_o saturates to the designed constant of 1.0mA. This was the desired outcome.

Q10. (10 Points)

Below is a graph of I_C , V_{CC} , V_E and the PSpice Schematic used to generate them.

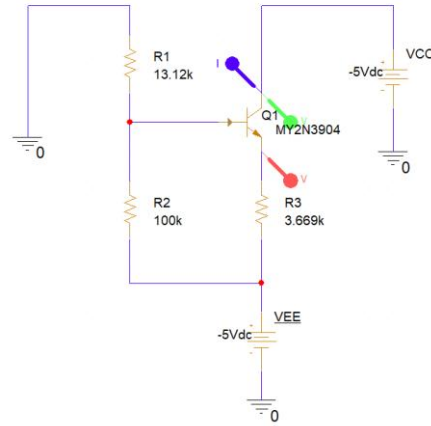


Fig 6. PSpice Schematic 2

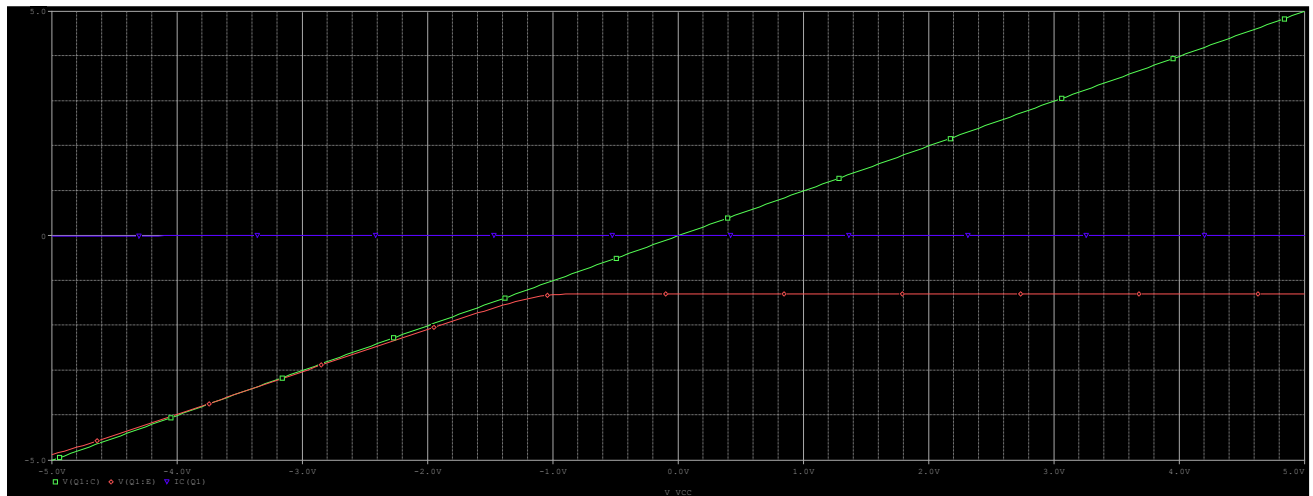


Fig 7. Characteristics 2

To determine $|V_{CE}|$, in Figure 7 we see that the BJT enters active mode at $V_E = -1.3114V$. The corresponding V_{CC} value at this point is $V_C = -1V$ (see Figure 8) thus

$$|V_{CE}| = V_{CC} - V_E = -1V - (-1.3114V) = 0.3114V$$

Since $|V_{CE}| \geq 0.3V$, this confirms that the BJT is operating in active mode.

Trace Color	Trace Name	Y1
	X Values	-1.0000
CURSOR 1,2	IC(Q1)	0.9958m
	V(Q1:C)	-1.0000
	V(Q1:E)	-1.3114

Fig 8. Voltage values